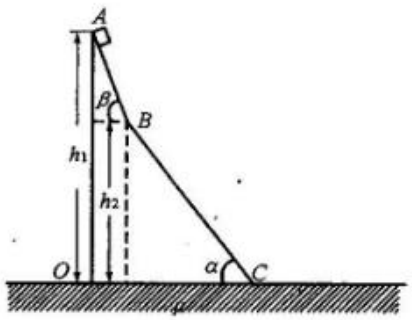


4. (25 points)

Here E is source emf (negligible internal resistance); R: resistance; S: switch. Right of A、B, 8 identical ideal capacitors, each C. From closing S to full charge, find the heat in R.
In your solution, mark on the diagram the assumed sign of charge on every capacitor plate.

